

Single Transistor Amplifier

Mario Alberto García-Ramírez, PhD

MU-JTSU JI

June 14, 2017

Amplification


Transistor as an amplifier

Intro

- ▶ Previously, we applied the input signal either to the base or gate and the output was taken from collector or drain
- ▶ By considering that both transistors have 3-terminals, we can “only” use collector & emitter or drain & source to get the signal
- ▶ As before, we’re going to use the same 4-resistor configuration, coupling and by-pass capacitors are also used to modify the signal input/output as well as the ac characteristics

Input/Output signals at BJT

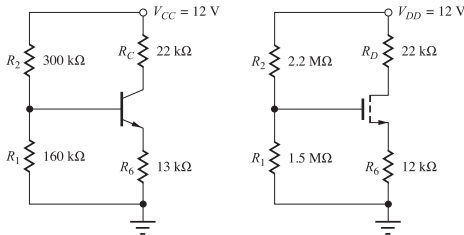- ▶ Large signal model for BJT allow us to know where the input signal for a forward bias BJT is



$$i_C = I_S \left[\exp \left(\frac{v_{BE}}{V_T} \right) \right] \quad i_B = \frac{i_C}{\beta_F} = \frac{I_S}{\beta_F} \left[\exp \left(\frac{v_{BE}}{V_T} \right) \right]$$
$$i_E = \frac{I_S}{\alpha_F} \left[\exp \left(\frac{v_{BE}}{V_T} \right) \right]$$


- ▶ To increase ' I_S ' quite a bit, we also need to increase v_{BE} as $v_{BE} = v_B - v_E$
- ▶ A signal needs to be added to base or emitter, collector has no effect whatsoever in terminal currents

Input/Output signals at BJT


- ▶ By increasing I_C & I_E create larger voltages across R_C and R_E
- ▶ As i_B is a β factor smaller than i_C or i_E , base is not used for output signal
- ▶ As for the FET, $i_S = i_D = \frac{K_n}{2}(v_{GS} - V_{TN})^2$ and $i_G = 0$
- ▶ To vary significantly I_S , v_{GS} need to change as $v_{GS} = v_G - v_S$
- ▶ Input signal can be injected through gate or source at FET
- ▶ By varying drain voltage, has a minor effect on terminal currents ($\lambda \neq 0$), ergo drain is not appropriate for signal injection
- ▶ On the other hand, gate terminal is not used as output terminal due to $i_G = 0$
- ▶ There are 3-main families of amplifiers:
Common-Emitter/Common-Source (C-E/C-S),
Common-Base/Common-Gate (C-B/C-G) and
Common-Collector/Common-Drain (C-C/C-D)

Common-Emitter/Common-Source (C-E/C-S)

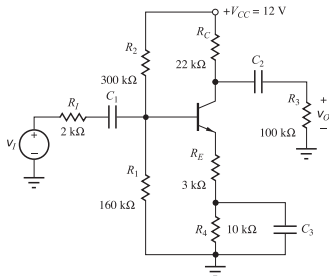
- In those diagrams R_6 has been divided between R_4 and C_2




(a)

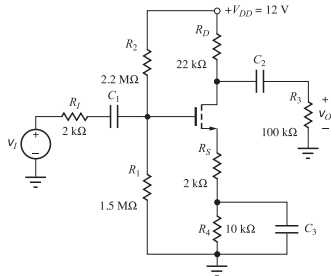

(b)

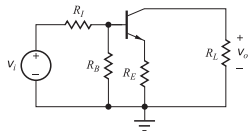




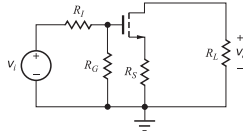
(c) $R_B = R_1 \parallel R_2$ $R_E = R_C \parallel R_3$



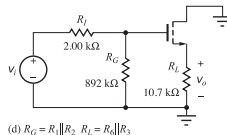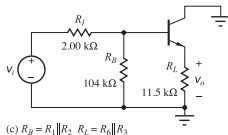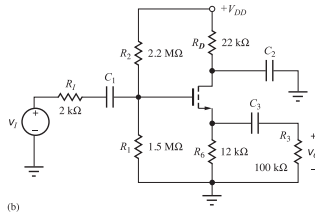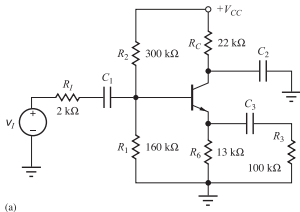(d) $R_G = R_1 \parallel R_2$ $R_L = R_D \parallel R_3$


Common-Collector/Common-Drain (C-C/C-D)

- ▶ In here signals are injected into the base/gate and the output is in emitter or source
- ▶ Collector/drain are bypassed by C_2
- ▶ C-C & C-D amplifiers pride a voltage gain ≈ 1 , moreover, input signals can be fairly large without exceeding the small-signal limits




Common-Base/Common-Gate (C-B/C-G)

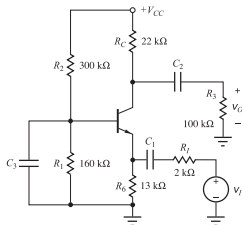
- ▶ *ac* signals are injected into the emitter/source and extracted from the collector/drain
- ▶ Base/gate terminals are bypassed by C_2 , those are common connections between input/output ports
- ▶ It shows a voltage gain at much lower input resistance




(a)

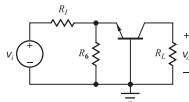

$$(c) R_L = R_C \parallel R_3$$

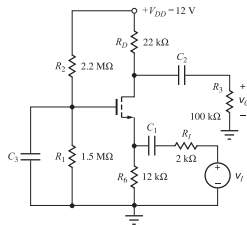


(b)

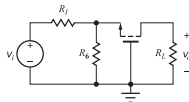


$$(d) R_L = R_D \parallel R_3$$



Common-Emitter Amplifier

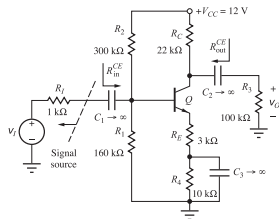

(a)

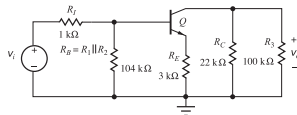


(b)

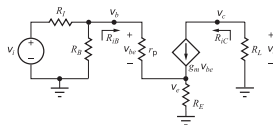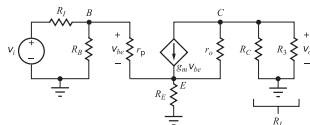

- ▶ We consider that we found Q-point and values for I_C and V_{CE} and $R_B = R_1 \parallel R_2$, R_4 is eliminated due to C_3 and $R_L = R_C \parallel R_3$
- ▶ NOTE: r_o is removed due to we already know ;)

Common-Emitter Amplifier

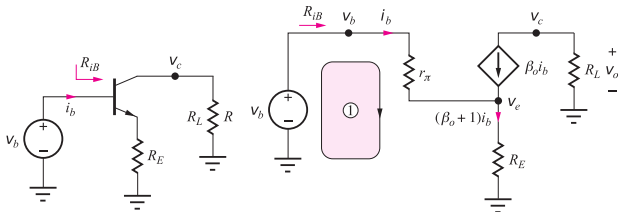

- ▶ Terminal voltage gain is defined as

$$A_v^{CE} = \frac{v_o}{v_i} = \left(\frac{v_o}{v_b} \right) \left(\frac{v_b}{v_i} \right) = A_v^{CE} \left(\frac{v_b}{v_i} \right) \text{ where } A_{vt}^{CE} = \left(\frac{v_c}{v_b} \right)$$

- ▶ as $v_c = -\beta_o i_b R_L$, we've got that

$$A_{vt}^{CE} = \frac{v_c}{V_b} = -\frac{\beta_o R_L}{r_\pi + (\beta_o + 1)R_E} \approx -\frac{g_m R_L}{1 + g_m R_E}$$

where $\beta_o \gg 1$ and $\beta_o = g_m r_\pi$

Common-Emitter Amplifier

- ▶ The input resistance is defined as

$$R_{iB} = \frac{v_b}{i_b} = r_\pi + (\beta_0 + 1)R_E \approx r_\pi(1 + g_m R_E)$$

- ▶ The overall input resistance $R_{in}^{CE} = R_B \parallel R_{iB}$
- ▶ The voltage gain of the amplifier, that includes the source resistance, the v_b at the BJT is

$$v_b = v_i \frac{R_B \parallel R_{iB}}{R_I + (R_B \parallel R_{iB})}$$

- ▶ As a result of the above equations, the total voltage gain is defined as

$$A_v^{CE} = A_v^{CE} \left(\frac{v_b}{v_i} \right) = - \left(\frac{g_m R_L}{1 + g_m R_E} \right) \left[\frac{R_B \parallel R_{iB}}{R_I + (R_B \parallel R_{iB})} \right]$$

Common-Emitter Amplifier

- ▶ If we consider that the source resistance is small $R_I \ll R_B \parallel R_{iB}$, we've $A_v^{CE} = A_{vt}^{CE} = -\frac{g_m R_L}{1 + g_m R_E}$
- ▶ In order to get a large signal as possible we consider a zero resistance at emitter $R_E = 0$ $A_v^{CE} \approx -g_m R_L = -g_m (R_C \parallel R_3)$ and $A_v^{CE} \approx -10 V_{CC}$
- ▶ To amplify the condition for voltage at emitter is:
$$v_e = (\beta_0 + 1) i_b R_E = \frac{(\beta_0 + 1) R_E}{r_\pi + (\beta_0 + 1) R_E} v_b \approx \frac{g_m R_E}{1 + g_m R_E} v_b \approx v_b$$
- ▶ As for current $i_E \approx \frac{v_b}{R_E}$, $v_0 = -i_c R_L = -\alpha_0 i_e R_L \approx -i_e R_L$,
ergo $A_{vt}^{CE} = -\frac{g_m R_L}{1 + g_m R_E} \approx -\frac{R_L}{R_E}$

Common-Emitter Amplifier


- ▶ Resistance at the BJT collector R_{iC} is defined by $R_{th} = R_B \parallel R_I$, ergo $R_{iC} = r_0 \left(1 + \frac{\beta_0 R_E}{R_{th} + r_\pi + R_E} \right) + (R_{th} + r_\pi) \parallel R_E \approx r_0 \left(1 + \frac{\beta_0 R_E}{R_{th} + r_\pi + R_E} \right)$ by having a few considerations we've got

$$R_{iC} \approx r_0 [1 + g_m (R_E \parallel r_\pi)] = r_0 + \mu_f (R_E \parallel r_\pi)$$


- ▶ The output resistance is defined as

$$R_{out}^{CE} = R_C \parallel R_{iC} = R_C \parallel r_0 \left(1 + \frac{\beta_0 R_E}{R_{th} + r_\pi + R_E} \right)$$



Common-Source Amplifier

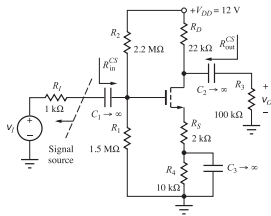

(a)

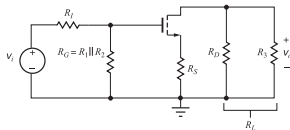

(b)

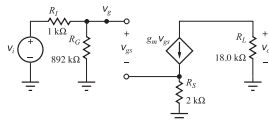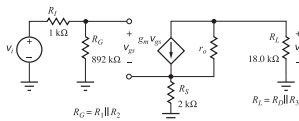

- ▶ In a similar way as for the previous configuration we've got that the source voltage gain is $A_{vt}^{CS} = -\frac{g_m R_L}{1 + g_m R_S}$
- ▶ The Common-Source voltage gain general expression is defined as $A_v^{CS} = -\frac{g_m R_L}{1 + g_m R_S} \left(\frac{R_G}{R_G + R_I} \right)$

Common-Source Amplifier

- ▶ Gain for large R_S $A_{vt}^{CS} = -\frac{g_m R_L}{1 + g_m R_S} \approx -\frac{R_L}{R_S}$
- ▶ When there is a low resistance at source
 $A_v^C \approx -g_m R_L = -g_m (R_D \parallel R_3)$
- ▶ The common-source output resistance is defined as
 $R_{out}^{CS} = R_D \parallel R_{iD} = R_D \parallel r_0(1 + g_m R_S) \approx R_D$

Common-Collector Amplifier


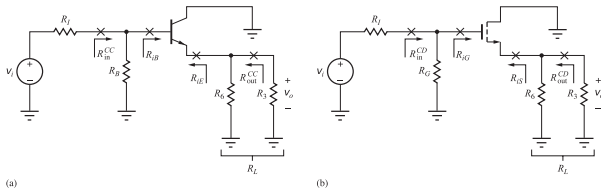


Figure 14.15 (a) ac equivalent circuit for the C-C amplifier. (b) ac equivalent circuit for the C-D amplifier.

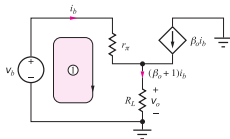

- ▶ The voltage gain is defined as $v_o = (\beta_0 + 1)i_b R_L$, where $R_L = R_3 \parallel R_6$
- ▶ the input current is related to the applied voltage as $v_b = i_b r_\pi + (\beta_0 + 1)i_b R_L = i_b [r_\pi + (\beta_0 + 1)R_L]$

Common-Source Amplifier

- ▶ The input resistance is defined as

$$R_{iB} = \frac{v_b}{i_b} = r_\pi + (\beta_0 + 1)R_L \approx r_\pi(1 + g_m R_L)$$


- ▶ As for R_{in} , we've $R_{in}^{CC} = R_B \parallel R_{iB} = R_B \parallel r_\pi(1 + g_m R_L)$, where $R_L = R_6 \parallel R_3$
- ▶ The overall gain voltage is defined as

$$A_v^{CC} = A_{vt}^{CC} \left[\frac{R_B \parallel R_{iB}}{R_I + (R_B \parallel R_{iB})} \right]$$

- ▶ for the MOSFET it is $A_v^{CC} = A_{vt}^{CC} \left(\frac{v_b}{v_i} \right)$ ergo,

$$A_v^{CC} = A_{vt}^{CC} \left(\frac{R_G}{R_I + R_G} \right)$$

Common-Source Amplifier

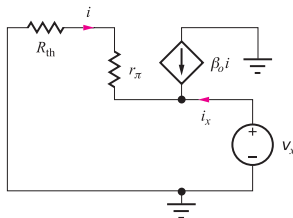

$$R_{iE} = \frac{v_x}{i_x}$$


- ▶ The output resistance is defined as

$$i_x = -i - \beta_0 i = \frac{v_x}{r_{\pi} + R_{th}} - \beta_0 \left(-\frac{v_x}{r_{\pi} + R_{th}} \right), \text{ rearranging terms}$$


$$R_{iE} = \frac{r_{\pi} + R_{th}}{\beta_0 + 1} \approx g_m^{-1} + R_{th} \beta_0^{-1}, \text{ fixing the terms and}$$

considering that $\beta_0 \gg 1$ $R_{iS} = g_m^{-1}$
- ▶ The current gain is defined as $A_{it}^{CC} = \frac{i_1}{i} = \beta_0 + 1$ and $A_{it}^{CD} = \infty$


Multistage ac Coupled Amplifiers

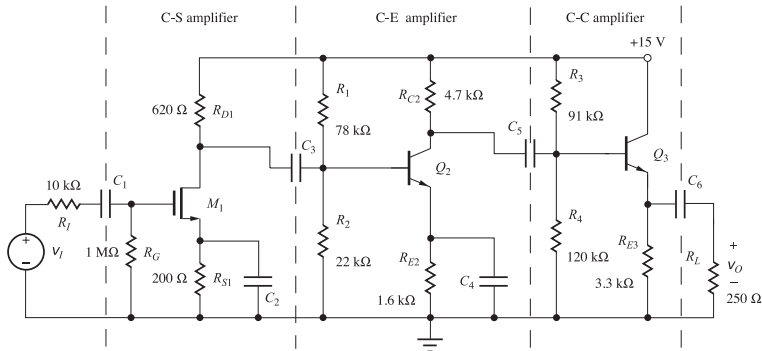

Multistage ac Coupled Amplifiers

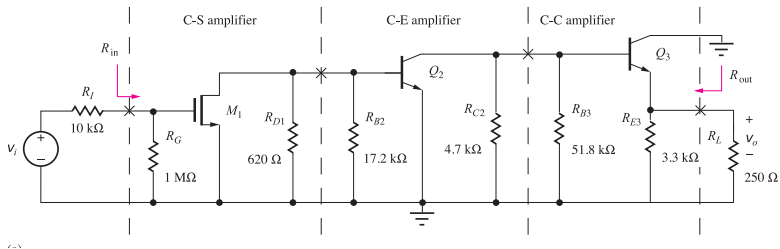

Multistage ac Coupled Amplifiers

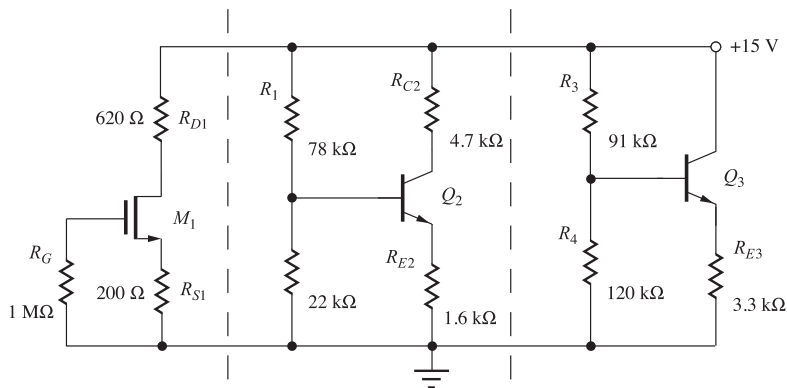

Common-Source Amplifier

- ▶ In this example, C_1 , C_3 , C_5 , and C_6 are coupling capacitors that provide dc isolation between stages
- ▶ It allows independent design of the bias circuitry
- ▶ C_2 and C_4 are bypass capacitors that are used to get the highest voltage gain from both configurations
- ▶ First stage is as CS amp, it has a high input impedance with high voltage gain, second stage is a CE amp, it gives high voltage gain and the third is a voltage follower, it has low output resistance
- ▶ According to:
 $M_1: K_n = 10 \text{ mA/V}^2, V_{TN} = -2 \text{ V}, \lambda = 0.02 \text{ V}^{-1}$
 $Q_2: \beta_F = 150, V_A = 80 \text{ V}, V_{BE} = 0.7 \text{ V}$
 $Q_3: \beta_F = 80, V_A = 60 \text{ V}, V_{BE} = 0.7 \text{ V}$