
UM-SJTU JOINT INSTITUTE
ELECTRONIC CIRCUITS
(VE311)

LABORATORY REPORT

LAB 5: OP-AMPS

Name: Chao Junyu
Name: Liu Yihao

ID: 515370910206
ID: 515370910207

Date: 21 July 2017

Contents

1	Objectives	3
2	Experiment procedures	4
2.1	Simple amplifier	4
2.2	Filters	4
3	Experimental results and discussion	5
3.1	Simple amplifier	5
3.2	Filters	8
3.2.1	High-pass filter	8
3.2.2	Low-pass filter	9
4	Conclusion	10
5	Reference	10
5.1	References	10

1 Objectives

In this practice, the operational amplifier is going to be tested. Basically, it is the key applications for basic science. Whole set of equations, carrier mobility, Q-point, bias at triode, operation in either as a logic gate or amplification, among quite a few others lies within this device that as a matter of a bitter sweetness, it is another milestone for nowadays technology. The Op-Amp is basically a massive array of, among others quite a few transistors such as npn & pnp, diodes, resistors, capacitors (inductors are quite difficult to either reduce or pack with the others passive devices), sources, etc. Basically, it is the key applications for basic science. In Advance ask for which are the Op-Amps that the lab has or if possible use TL084 (old but works, very well).

2 Experiment procedures

2.1 Simple amplifier

The first circuit that we're going to test is a rather simple amplifier as shown in Figure 1.

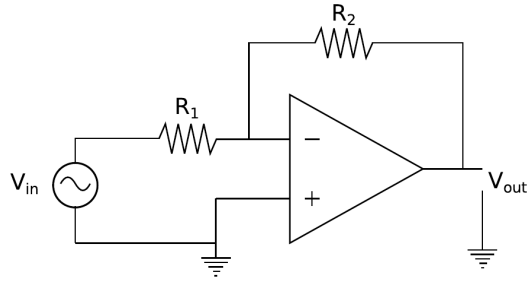


Figure 1: Basic configuration

The relationship that you're going to analyze is the amplification of a $V_{in} = 0.1$ V and the output should be: 1, 5, 10 and 20 V. For a separated experiment, change the source for a sinusoidal one with $V_{in} = 0.2$ V and output 10 V, with a frequency variation for 100 Hz, 500 Hz, 5 kHz, 100 kHz, 2 MHz, 10 MHz and 20 MHz.

2.2 Filters

For the second circuit, a filter or filters are in order to be analyzed, as shown in Figure 2(a) & 2(b) simulate and fabricated. Figure shows the diagram of the filter that is required to be analyzed.

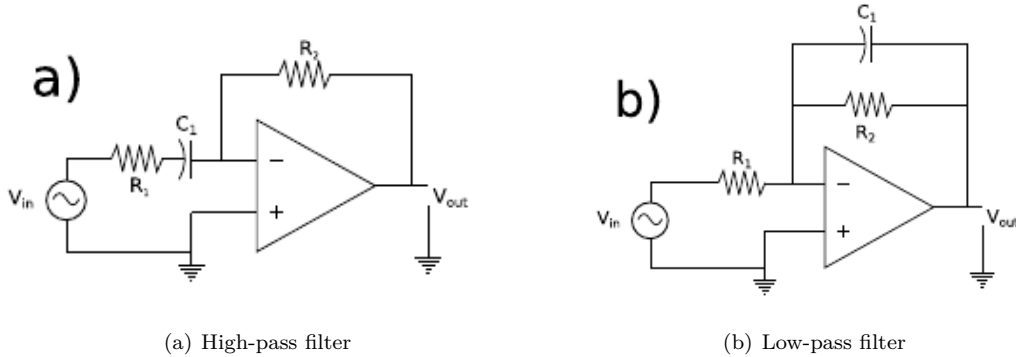


Figure 2: Basic configuration for active filters.

Calculate the right values for capacitors and resistors in order to get the follow cut-off frequencies: 2 kHz, 10 kHz and 1 MHz.

3 Experimental results and discussion

3.1 Simple amplifier

In order to get output of 1, 5, 10 and 20 V, we use $R_1 = 1\text{ k}\Omega$ and $R_2 = 1, 5, 10$ and $20\text{ k}\Omega$. The result was shown in Figure 3.



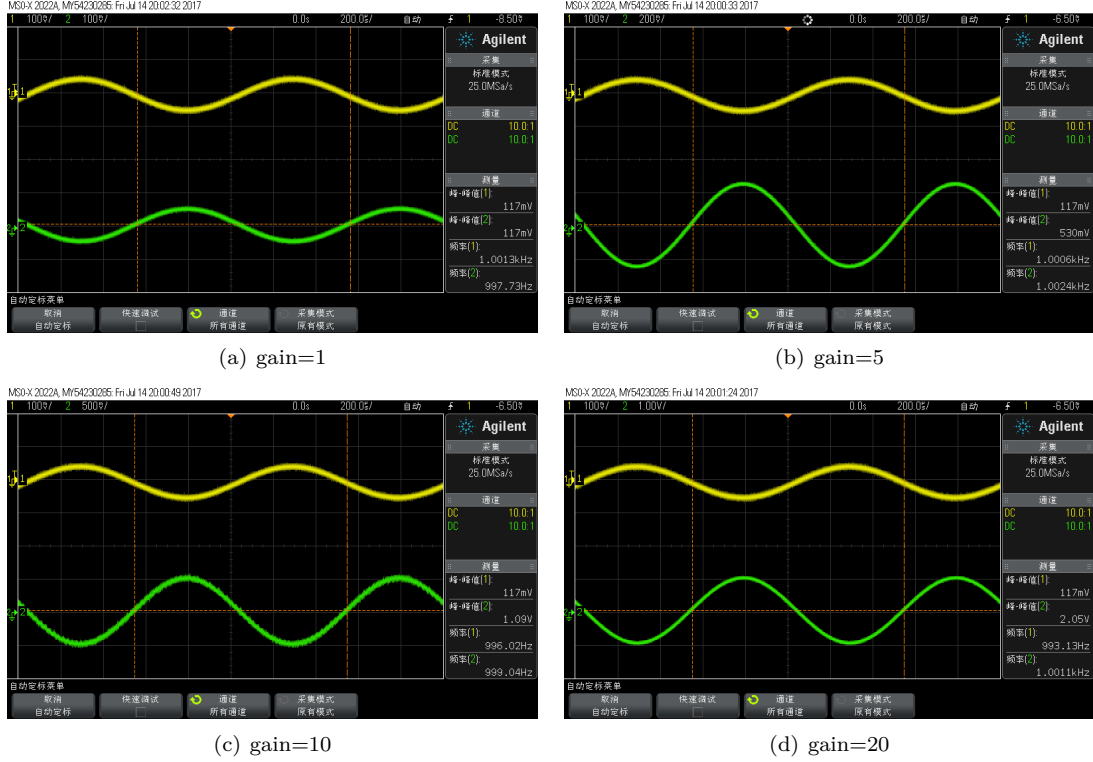


Figure 3: Analysis of amplification with different gain.

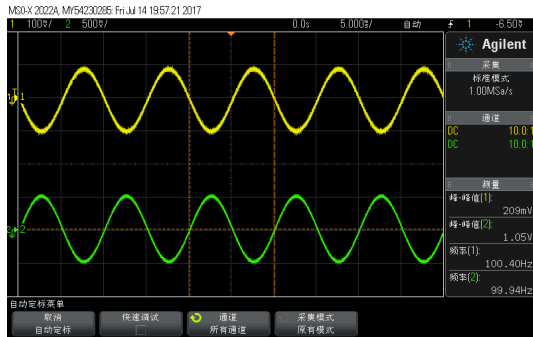
Change the source for a sinusoidal one with $V_{in} = 0.2\text{ V}$ and output 10 V , with a frequency variation for 100 Hz , 500 Hz , 5 kHz , 100 kHz , 2 MHz , 10 MHz and 20 MHz . The result was shown in Figure 4. The simulation result was shown in 5.




(a) 100 Hz

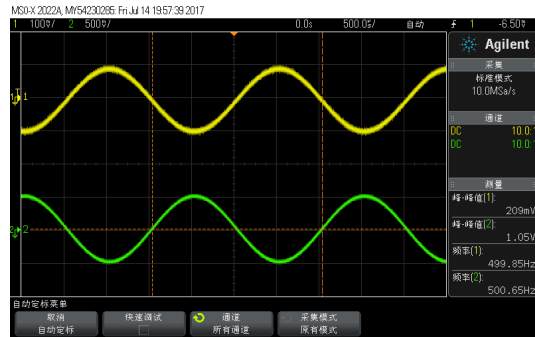


(b) 500 Hz

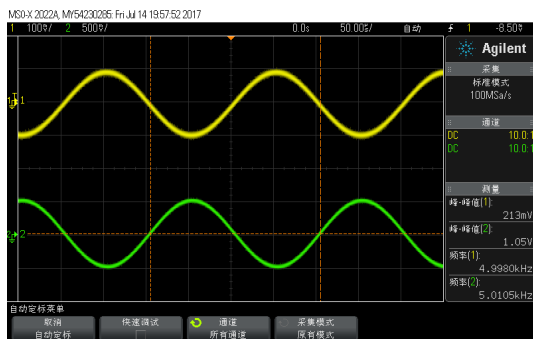


(c) 5 kHz

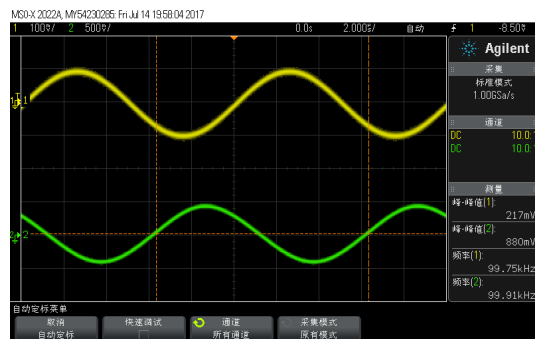


(d) 100 kHz

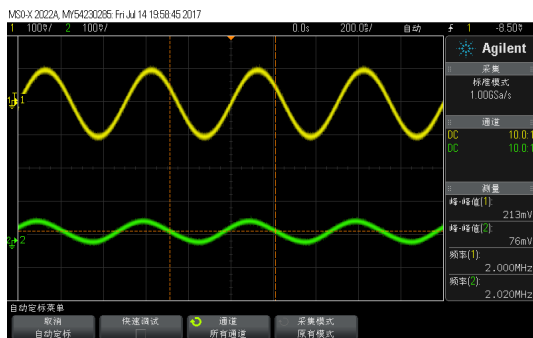

(e) 2 MHz

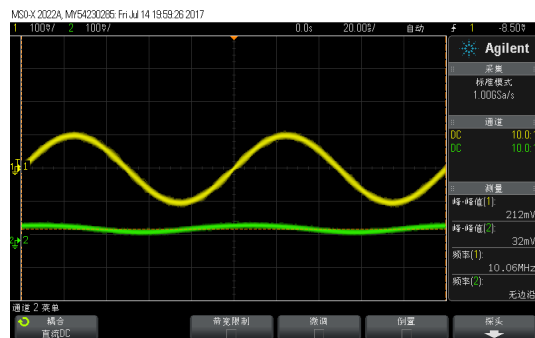


(f) 10 MHz

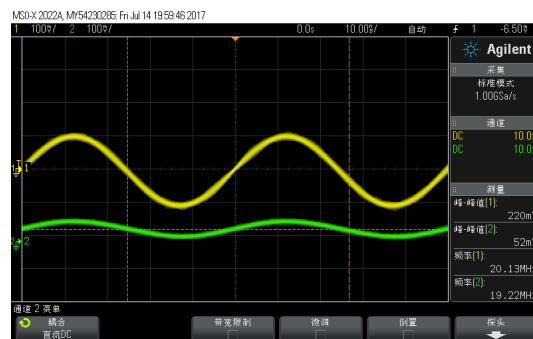


(g) 20 MHz


Figure 4: Analysis of amplification with different frequency.

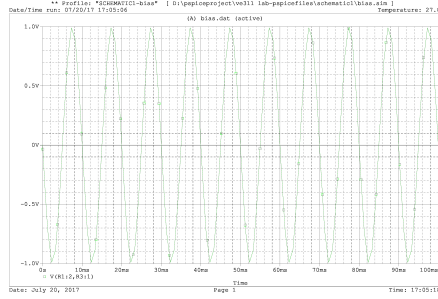


(a) 100 Hz

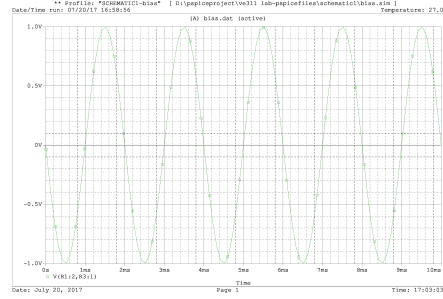


(b) 500 Hz

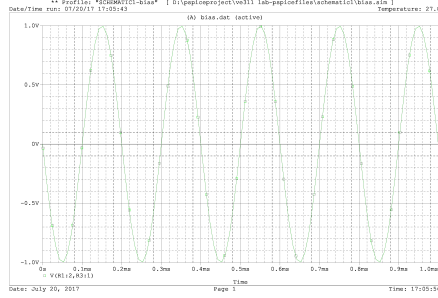


(c) 5 kHz

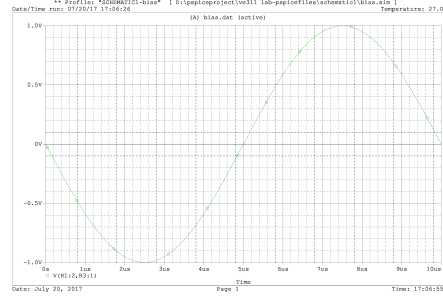


(d) 100 kHz

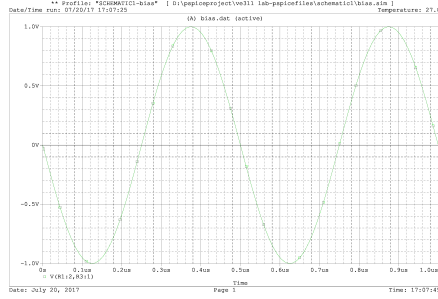

(e) 2 MHz

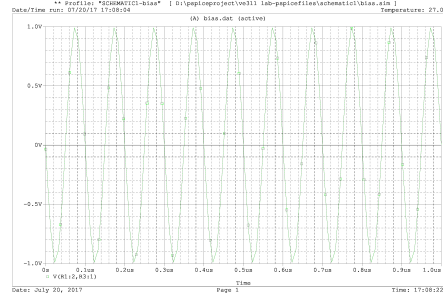

(f) 10 MHz

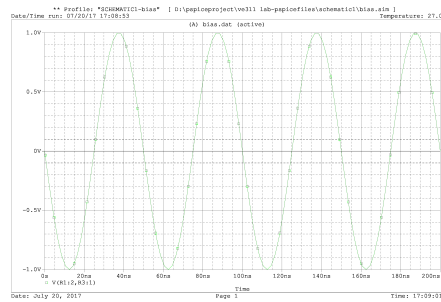

(g) 20 MHz

Figure 5: Simulation of amplification with different frequency.

3.2 Filters

When cut-off frequency is 2 kHz, and $R_1 = 1\text{ k}\Omega$, $R_2 = 5\text{ k}\Omega$, we can calculate the value of C .

3.2.1 High-pass filter

$$f = \frac{1}{2\pi R_1 C_1}$$

$C_1 \approx 79.5\text{ nF}$, the result was shown in Figure 6.

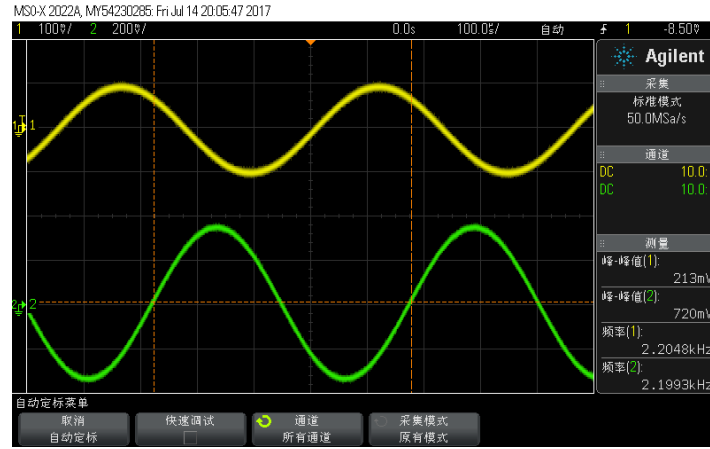


Figure 6: Analysis of high-pass filter

The simulation result was shown in Figure 7.

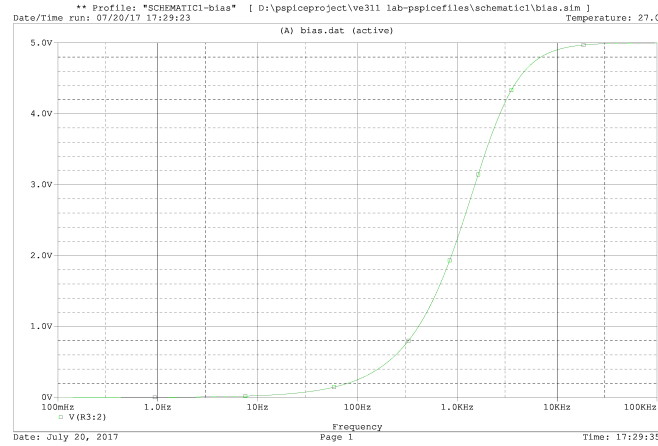


Figure 7: Simulation of high-pass filter

3.2.2 Low-pass filter

$$f = \frac{1}{2\pi R_2 C_2}$$

$C_2 \approx 15.9 \text{ nF}$, the result was shown in Figure 8.

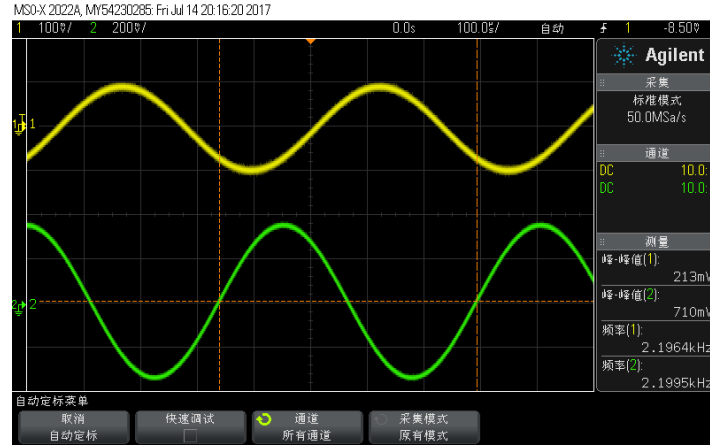


Figure 8: Analysis of low-pass filter

The simulation result was shown in Figure 9.

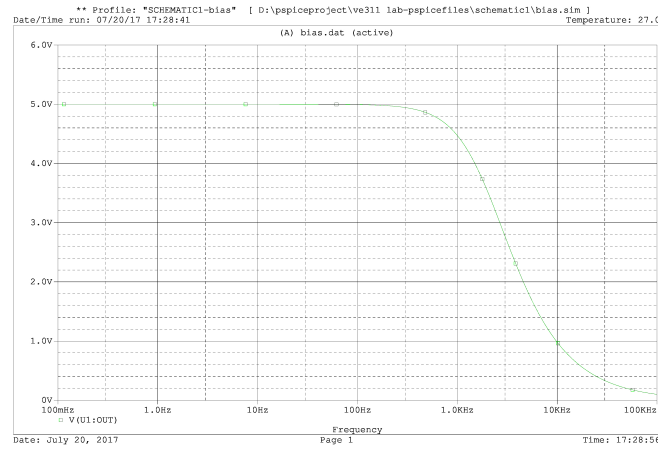


Figure 9: Simulation of low-pass filter

4 Conclusion

In the first part, we find the attributes of a simple amplifier.

In the second part, we find the relationship of cut-off frequency and resistors and capacitors.

5 Reference

5.1 References

1. Lab5 Manual