## Introduction to the **Dark Side** a.k.a.: *Electronics*

Mario Alberto García-Ramíez, PhD

MU-JTSU JI

April 30, 2017

### Introduction

Where do we need to start? Why?

#### Review

Nomenclature Series and Parallel Nets

Fantastic Four  $\approx$  ish Moving on  $\cdots$  on

Math

- Math
- Physics

- Math
- Physics
- ► High skills in programming

- Math
- Physics
- High skills in programming
- ► Those are the basics skills needed for this course. However, those are not enough or even the tip of the iceberg. Actually, do we need:

- Math
- Physics
- High skills in programming
- Those are the basics skills needed for this course. However, those are not enough or even the tip of the iceberg. Actually, do we need:
- ► Philosophy

- Math
- Physics
- High skills in programming
- Those are the basics skills needed for this course. However, those are not enough or even the tip of the iceberg. Actually, do we need:
- ► Philosophy
- ► Art

- Math
- Physics
- High skills in programming
- Those are the basics skills needed for this course. However, those are not enough or even the tip of the iceberg. Actually, do we need:
- ► Philosophy
- ► Art
- ▶ Literature

# Why those requirements are a milestone for us?

### THE Question!!!

Which is the main reason for the development of Science and Technology?

#### There are two main answers:

First one is based on **to know**. Why does it happened?, why this is occurring?, it is possible to see beyond?, it is possible to fly faster?, can we control our sun?, ...

The second one is quite vulgar. We need to do or to develop such technology to sell it. Do not take me wrong, it is ok to be greedy, everyone need a Tesla Model S, it is just a bit vulgar.

### Hands on... then

Electronics, nowadays, shape and is reshaping the world each single hour/day/minute.

It is divided in:

- Analog
- Digital
- Mix-Signal

Whole Electronics that we know, so far, are based on those. It worth to mention that, each one, despite to follow the same "rules", behave in a completely different manner and its applications have specific characteristics.

Go to the basics.

▶ Charge =  $1.602 \times 10^{-19}$  C

- ► Charge =  $1.602 \times 10^{-19}$  C
- ▶ Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s

- ▶ Charge =  $1.602 \times 10^{-19}$  C
- ► Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s
- ▶ Voltage = Ed (V)

- ▶ Charge =  $1.602 \times 10^{-19}$  C
- ► Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s
- ▶ Voltage = Ed (V)
- ► Ohm's law

$$I = V \times R(A)$$

- ▶ Charge =  $1.602 \times 10^{-19}$  C
- ► Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s
- ▶ Voltage = Ed (V)
- ► Ohm's law

$$I = V \times R(A)$$

Coulomb's Law

$$F=\frac{kq_1q_2}{r^2}(N)$$



- ▶ Charge =  $1.602 \times 10^{-19}$  C
- ► Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s
- ▶ Voltage = Ed (V)
- ► Ohm's law

$$I = V \times R(A)$$

Coulomb's Law

$$F=\frac{kq_1q_2}{r^2}(N)$$

Capacitance C = Q/V (C)

- ► Charge =  $1.602 \times 10^{-19}$  C
- ► Current = charges in movement  $\frac{dq(t)}{dt}$  → Amper = C/s
- ▶ Voltage = Ed (V)
- ▶ Ohm's law

$$I = V \times R(A)$$


Coulomb's Law

$$F=\frac{kq_1q_2}{r^2}(N)$$

- Capacitance C = Q/V (C)
- ▶ Power P = VI or  $I^2R$  or  $V^2/R$

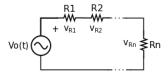
## Net Circuits: parallel and series

There are two main Net circuits: series and parallel. Series



In this configuration, current is the same in whole net but voltage. It changes by element.

#### Parallel

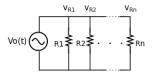


In this configuration, current varies according to each net but voltage is the same for all.

- Usually, electronic nets are a combination of series and parallel elements.
- ► The analysis for those has evolve and become a bit complex in order to solve such nets.
- ► There are two main methods to solve those circuits such as: Net analysis and node analysis.
- ► However, the key element to solve those is based on the experience and continue study.
- This is why, there is a "review" handout to solve a few problems.
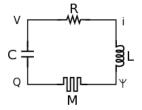
### Passive elements

In the beginning, there were three passive elements such as capacitance, resistance and inductance.

Those elements are linked one each other through the energy that drives i.e. R I  $\iff$  V, C V  $\iff$  Q, L I $\iff$   $\Psi$  as shown in Figure.



In the 1970s a scientist *Chua* theorised the existence of a passive element that can relate flux with charge... in early 2010 a team of Russian Scientist invented the first element known as **Memristor**.

# Complex Nets

In order to solve complex nets, it is required to have a basic knowledge on Maths, Physics and common sense. We are going to review the basic maths required to solve it accordingly. There are two main ways: **Impedances** and **Reactances** 

 Reactances: Inductive, Resistive and Capacitive Capacitive

$$\chi_C = \frac{1}{2\pi fC}$$

Inductive

$$\chi_L = 2\pi f L$$

Resistive

$$\chi_R = R$$

•  $\chi_C$  and  $\chi_L$  a frequency dependent but  $\chi_R$ 

- $\chi_C$  and  $\chi_L$  a frequency dependent but  $\chi_R$
- ▶ It means that, in order to "properly work" these devices, it is required to have a source variable in time.

- $\chi_C$  and  $\chi_L$  a frequency dependent but  $\chi_R$
- ▶ It means that, in order to "properly work" these devices, it is required to have a source variable in time.
- ▶ There are quite a few sources such as:  $\sin(\omega t + \theta)$ ,  $\cos(\omega t + \theta)$ , PWL, monostable, bistable, analog, digital, among many others.

- $\chi_C$  and  $\chi_L$  a frequency dependent but  $\chi_R$
- ▶ It means that, in order to "properly work" these devices, it is required to have a source variable in time.
- ▶ There are quite a few sources such as:  $\sin(\omega t + \theta)$ ,  $\cos(\omega t + \theta)$ , PWL, monostable, bistable, analog, digital, among many others.
- According to the device arrays and the source implemented, the obtained signal might behave as you wish if properly analysed or not.

- $\chi_C$  and  $\chi_L$  a frequency dependent but  $\chi_R$
- ▶ It means that, in order to "properly work" these devices, it is required to have a source variable in time.
- ▶ There are quite a few sources such as:  $sin(\omega t + \theta)$ ,  $cos(\omega t + \theta)$ , PWL, monostable, bistable, analog, digital, among many others.
- According to the device arrays and the source implemented, the obtained signal might behave as you wish if properly analysed or not.
- ► There are three main ways to "analyse" such nets: algebraically, numerically and by simulating it.

Whole the slides shown in here are just a basic review of the knowledge obtained by you through a set of lectures, homework, lab and personal experience. Besides those, I'll strongly suggest you to start reading the course book as well as other non-related to the class such as Chinese or International literature. As well as:

Algebra

- Algebra
- Basic Physics

- Algebra
- Basic Physics
- ▶ Numerical Analysis: Spice, Matlab, C/C++, Python...

- Algebra
- Basic Physics
- ▶ Numerical Analysis: Spice, Matlab, C/C++, Python...
- ► Have basic Common Sense

- Algebra
- Basic Physics
- ▶ Numerical Analysis: Spice, Matlab, C/C++, Python...
- Have basic Common Sense
- Develop a Open Mind

- Algebra
- Basic Physics
- ▶ Numerical Analysis: Spice, Matlab, C/C++, Python...
- Have basic Common Sense
- Develop a Open Mind
- Work, work, work, · · · Work Hard

- Algebra
- Basic Physics
- ▶ Numerical Analysis: Spice, Matlab, C/C++, Python...
- Have basic Common Sense
- Develop a Open Mind
- ▶ Work, work, work, · · · Work Hard
- ► The *MOST* important, **Enjoy the ride** or perish.