

# VE311 Electronic Circuits

## Homework 07

UM-SJTU JI

Shen Jiaqi

Zhang Xinwei

Mario Alberto García-Ramírez, PhD

The course homework is intended for the students to learn and to think rather than just copy and paste. This is why, me and my TAs team are confident that you're going to learn.

- Poles and Zeros


1. Solve the following set of equations and find if the system is stable or unstable. What is the frequency at -3dB? Use the plots of Bode and Nyquist and support your response. Mathematical development is required, magic does not exist.

$$F_L(s) = \frac{s(s + 10)}{(s + 100)(s + 25)}$$


$$F_H(s) = \frac{1 - \frac{s}{10^5}}{(1 + \frac{s}{10000})(1 + \frac{s}{40000})}$$

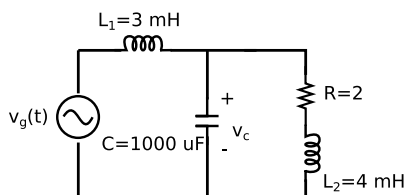2. Solve the following circuits and interpret the result if those are stable or unstable through Bode and Nyquist diagrams. Magic only exists in Hogwarts... and even there you've to study...

In the following circuit, the output voltage is referred to the inductor for a  $v_g(t) = 10 \sin(277t)$



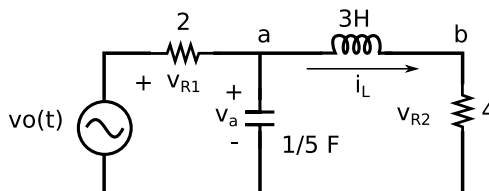For the following circuit, the output voltage is analyzed at resistor  $R_2 = 4\Omega$ . The applied voltage is  $v_0(t) = \frac{\pi t}{2}$ . And yes, this is a variable source. So enjoy!!!



3. For the next circuit, derive the expressions for  $V_1/V_i$ ,  $V_2/V_1$ ,  $V_0/V_i$ . Calculate the poles and zeros, obtain the bode diagram and compare it with a simulation in Spice, explain..., *if* (**PLEASE: PAY ATTENTION HERE!!!!!!**)  $R = 10\text{ k}\Omega$ ,  $C_1 = 20\text{ }\mu\text{F}$ ,  $R_1 = 10\text{ k}\Omega$ ,  $C_2 = 4.7\text{ mF}$  and  $R_f = 100\text{ k}\Omega$   $V_i = 100\cos(600t)$

