


# VE311 Homework 5

Liu Yihao 515370910207

## Problem 1.

First we should apply dc analysis to the circuit, it can be divided into three circuits.

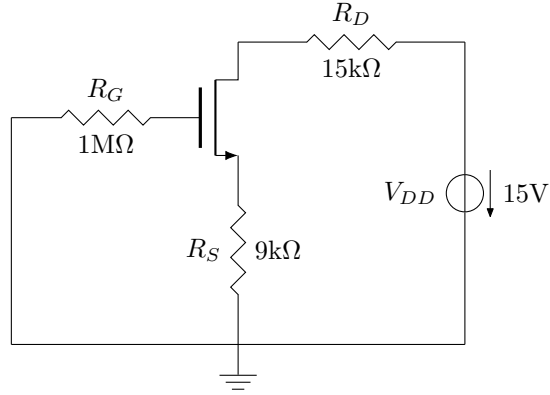(1) For  $M_1$ , the dc equivalent circuit is



According to the equations,

$$I_D = \frac{K_n}{2}(V_{GS} - V_{TN})^2$$
$$V_{GS} + I_D R_s = 0$$


We can get

$$V_{GS} + \frac{K_n R_s}{2}(V_{GS} - V_{TN})^2 = 0$$
$$V_{GS} = V_{TN} = \frac{1}{K_n R_s} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right)$$
$$I_D = \frac{1}{2K_n R_s^2} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right)^2$$
$$= \frac{1}{2 \cdot 0.3 \text{ A/V}^2 \cdot (9 \text{ k}\Omega)^2} \left( \sqrt{1 - 2 \cdot 0.3 \text{ A/V}^2 \cdot 9 \text{ k}\Omega \cdot -3 \text{ V}} - 1 \right)^2$$
$$\approx 0.33 \text{ mA}$$
$$V_{DS} = V_{DD} - I_D(R_D + R_S) = 15 \text{ V} - 0.33 \text{ mA} \cdot (15 \text{ k}\Omega + 9 \text{ k}\Omega) = 7.08 \text{ V}$$

$$\begin{aligned}
V_{GS} - V_{TN} &= \frac{1}{K_n R_s} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right) \\
&= \frac{1}{2 \cdot 0.3 \text{ A/V}^2 \cdot 9 \text{ k}\Omega} \left( \sqrt{1 - 2 \cdot 0.3 \text{ A/V}^2 \cdot 9 \text{ k}\Omega \cdot -3 \text{ V}} - 1 \right) \\
&= 0.023 \text{ V} < V_{DS}
\end{aligned}$$

So the  $Q$  point is (0.33 mA, 0.023 V), and it is in the saturated region.

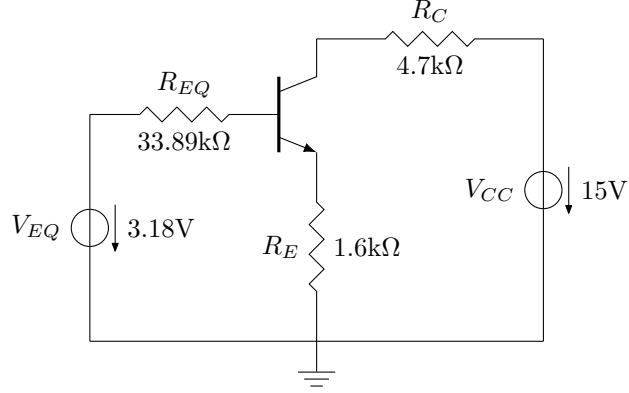(2) For  $Q_1$ , the dc equivalent circuit is



Suppose  $V_{BE} = 0.7\text{V}$ ,


$$I_C = \frac{V_{EQ} - V_{BE}}{\frac{R_{EQ}}{\beta_F} + \frac{\beta_F + 1}{\beta_F} R_E} = \frac{3.18 \text{ V} - 0.7 \text{ V}}{\frac{33.89 \text{ k}\Omega}{17} + \frac{17 + 1}{17} \cdot 1.6 \text{ k}\Omega} \approx 0.673 \text{ mA}$$

$$I_E = \frac{V_{EQ} - V_{BE}}{\frac{R_{EQ}}{\beta_F + 1} + R_E} = \frac{3.18 \text{ V} - 0.7 \text{ V}}{\frac{33.89 \text{ k}\Omega}{17 + 1} + 1.6 \text{ k}\Omega} \approx 0.712 \text{ mA}$$


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 15 \text{ V} - 0.673 \text{ mA} \cdot 4.7 \text{ k}\Omega - 0.712 \text{ mA} \cdot 1.6 \text{ k}\Omega \approx 10.70 \text{ V}$$

So the  $Q$  point is (0.673 mA, 10.70 V).

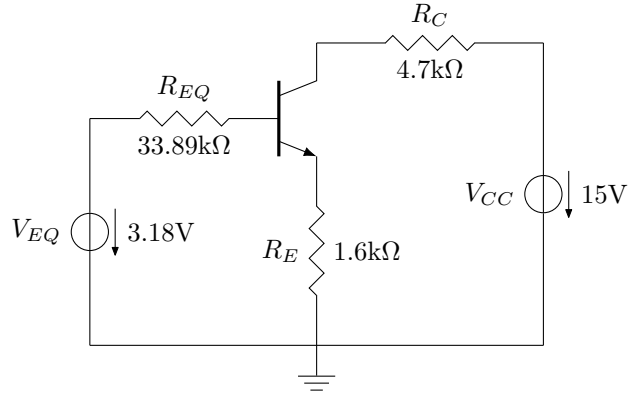(3) For  $Q_2$ , the dc equivalent circuit is



## Problem 2.

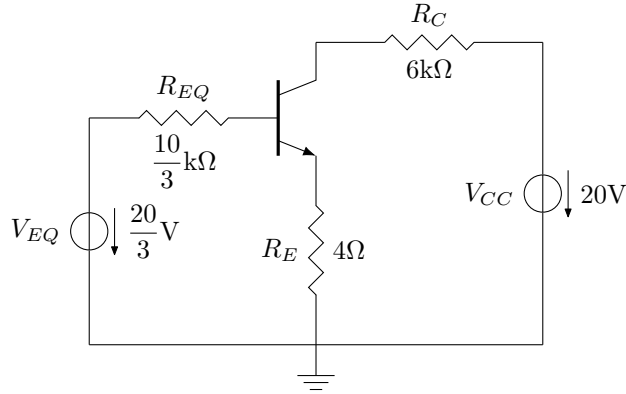

Suppose  $V_{BE} = 0.7\text{V}$ ,


$$I_C = \frac{V_{EQ} - V_{BE}}{\frac{R_{EQ}}{\beta_F} + \frac{\beta_F + 1}{\beta_F} R_E} = \frac{20/3\text{ V} - 0.7\text{ V}}{\frac{10/3\text{ k}\Omega}{75} + \frac{75 + 1}{75} \cdot 4\text{ k}\Omega} \approx 1.456\text{ mA}$$

$$I_E = \frac{V_{EQ} - V_{BE}}{\frac{R_{EQ}}{\beta_F + 1} + R_E} = \frac{20/3\text{ V} - 0.7\text{ V}}{\frac{10/3\text{ k}\Omega}{75 + 1} + 4\text{ k}\Omega} \approx 1.475\text{ mA}$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E = 20\text{ V} - 1.456\text{ mA} \cdot 6\text{ k}\Omega - 1.475\text{ mA} \cdot 4\text{ k}\Omega = 5.364\text{ V}$$

So the  $Q$  point is  $(1.456\text{ mA}, 5.364\text{ V})$ .

## Problem 3.

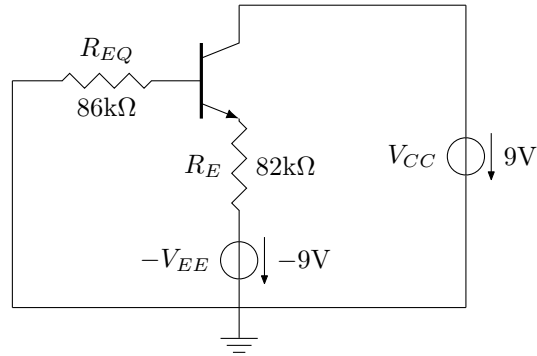

Suppose  $V_{BE} = 0.7\text{V}$ ,


$$I_E = \frac{V_{EE} - V_{BE}}{R_E} = \frac{9\text{ V} - 0.7\text{ V}}{82\text{ k}\Omega} \approx 101\text{ }\mu\text{A}$$

$$I_C = \frac{\beta_F}{\beta_F + 1} I_E = \frac{100}{100 + 1} \cdot 100\text{ }\mu\text{A}$$

$$V_{CE} = V_{CC} - I_C R_C - (-V_{BE}) = 9\text{ V} + 0.7\text{ V} = 9.7\text{ V}$$

So the  $Q$  point is  $(100\text{ }\mu\text{A}, 9.7\text{ V})$ .

### Problem 4.

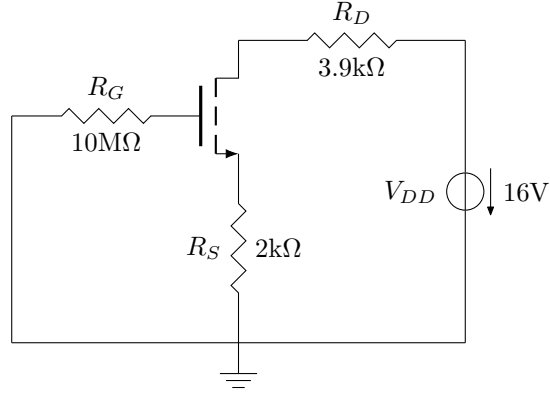

According to the equations,

$$I_D = \frac{K_n}{2}(V_{GS} - V_{TN})^2$$

$$V_{GS} + I_D R_s = 0$$

We can get

$$V_{GS} + \frac{K_n R_s}{2}(V_{GS} - V_{TN})^2 = 0$$

$$V_{GS} = V_{TN} = \frac{1}{K_n R_s} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right)$$

$$\begin{aligned} I_D &= \frac{1}{2K_n R_s^2} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right)^2 \\ &= \frac{1}{2 \cdot 400 \mu\text{A}/\text{V}^2 \cdot (2 \text{ k}\Omega)^2} \left( \sqrt{1 - 2 \cdot 400 \mu\text{A}/\text{V}^2 \cdot 2 \text{ k}\Omega \cdot -5 \text{ V}} - 1 \right)^2 \\ &= 1.25 \text{ mA} \end{aligned}$$


$$V_{DS} = V_{DD} - I_D(R_D + R_S) = 16 \text{ V} - 1.25 \text{ mA} \cdot (3.9 \text{ k}\Omega + 2 \text{ k}\Omega) = 8.625 \text{ V}$$

$$\begin{aligned} V_{GS} - V_{TN} &= \frac{1}{K_n R_s} \left( \sqrt{1 - 2K_n R_s V_{TN}} - 1 \right) \\ &= \frac{1}{2 \cdot 400 \mu\text{A}/\text{V}^2 \cdot 2 \text{ k}\Omega} \left( \sqrt{1 - 2 \cdot 400 \mu\text{A}/\text{V}^2 \cdot 2 \text{ k}\Omega \cdot -5 \text{ V}} - 1 \right) \\ &= 1.25 \text{ V} < V_{DS} \end{aligned}$$

So the  $Q$  point is (1.25 mA, 8.625 V), and it is in the saturated region.
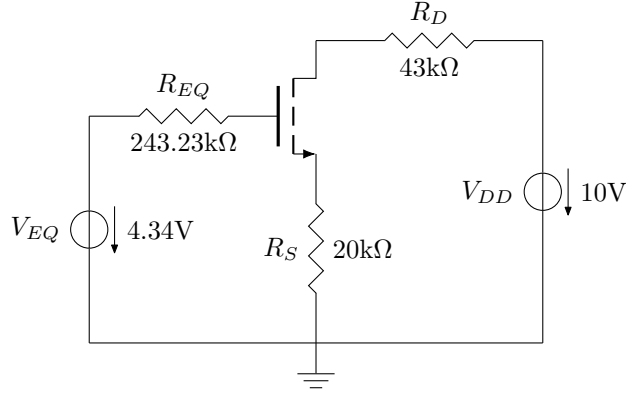
### Problem 5.

First, we draw the dc equivalent circuit:



According to the equations,

$$I_D = \frac{K_n}{2}(V_{GS} - V_{TN})^2$$

$$V_{GS} + I_D R_s = V_{EQ}$$

We can get

$$V_{GS} + \frac{K_n R_s}{2}(V_{GS} - V_{TN})^2 = V_{EQ}$$


$$V_{GS} = V_{TN} + \frac{1}{K_n R_s} \left( \sqrt{1 + 2K_n R_s (V_{EQ} - V_{TN})} - 1 \right)$$

$$\begin{aligned} I_D &= \frac{1}{2K_n R_s^2} \left( \sqrt{1 + 2K_n R_s (V_{EQ} - V_{TN})} - 1 \right)^2 \\ &= \frac{1}{2 \cdot 0.5 \text{ mA/V}^2 \cdot (20 \text{ k}\Omega)^2} \left( \sqrt{1 + 2 \cdot 0.5 \text{ mA/V}^2 \cdot 20 \text{ k}\Omega \cdot (4.34 \text{ V} - 1 \text{ V})} - 1 \right)^2 \\ &\approx 131 \mu\text{A} \end{aligned}$$

$$V_{DS} = V_{DD} - I_D (R_D + R_S) = 10 \text{ V} - 131 \mu\text{A} \cdot (43 \text{ k}\Omega + 20 \text{ k}\Omega) \approx 1.75 \text{ V}$$

$$\begin{aligned} V_{GS} - V_{TN} &= \frac{1}{K_n R_s} \left( \sqrt{1 + 2K_n R_s (V_{EQ} - V_{TN})} - 1 \right) \\ &= \frac{1}{0.5 \text{ mA/V}^2 \cdot 20 \text{ k}\Omega} \left( \sqrt{1 + 2 \cdot 0.5 \text{ mA/V}^2 \cdot 20 \text{ k}\Omega \cdot (4.34 \text{ V} - 1 \text{ V})} - 1 \right) \\ &\approx 0.717 \text{ V} < V_{DS} \end{aligned}$$

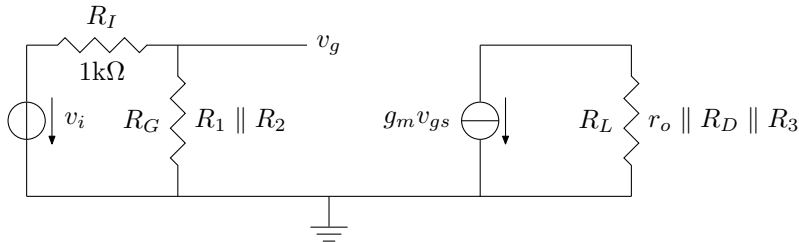So the  $Q$  point is  $(131 \mu\text{A}, 1.75 \text{ V})$ , and it is in the saturated region. Then we can draw the ac equivalent circuit:



$$\begin{aligned}
g_m &= \frac{2I_D}{V_{GS} - V_{TN}} = \frac{2 \cdot 131 \mu\text{A}}{0.717 \text{ V}} \approx 3.65 \times 10^{-4} \Omega^{-1} \\
r_o &= \frac{\frac{1}{\lambda} + V_{DS}}{I_D} = \frac{\frac{1}{0.0133 \text{ V}^{-1}} + 1.75 \text{ V}}{131 \mu\text{A}} \approx 587 \text{ k}\Omega \\
R_G &= R_1 \parallel R_2 \approx 243.23 \text{ k}\Omega \\
R_L &= r_o \parallel R_D \parallel R_3 \approx 28.6 \text{ k}\Omega
\end{aligned}$$

The voltage gain is

$$\begin{aligned}
A_v^{CS} &= -g_m R_L \left( \frac{R_G}{R_G + R_I} \right) \\
&= -3.65 \times 10^{-4} \Omega^{-1} \cdot 28.6 \text{ k}\Omega \cdot \left( \frac{243.23 \text{ k}\Omega}{243.23 \text{ k}\Omega + 1 \text{ k}\Omega} \right) \\
&\approx -10.4 \text{ dB}
\end{aligned}$$

## Problem 6.

(a)

$$\begin{aligned}
g_d &= \frac{I_S}{V_T} \exp\left(\frac{V_D}{V_T}\right) = \frac{8 \text{ fA}}{0.025 \text{ V}} \exp\left(\frac{0.6 \text{ V}}{0.025 \text{ V}}\right) \approx 8.48 \times 10^{-3} \Omega^{-1} \\
r_d &= \frac{1}{g_d} = \frac{1}{8.48 \times 10^{-3} \Omega^{-1}} \approx 118 \Omega
\end{aligned}$$

(b)

$$\begin{aligned}
g_d &= \frac{I_S}{V_T} \exp\left(\frac{V_D}{V_T}\right) = \frac{8 \text{ fA}}{0.025 \text{ V}} \exp\left(\frac{0 \text{ V}}{0.025 \text{ V}}\right) \approx 3.2 \times 10^{-13} \Omega^{-1} \\
r_d &= \frac{1}{g_d} = \frac{1}{3.2 \times 10^{-13} \Omega^{-1}} \approx 3.125 \times 10^{12} \Omega
\end{aligned}$$

(c)

$$\begin{aligned}
g_d &= \frac{I_S}{V_T} \exp\left(\frac{V_D}{V_T}\right) = \frac{1}{r_d} \\
V_D &= V_T \ln\left(\frac{V_T}{I_S r_d}\right) = 0.025 \text{ V} \ln\left(\frac{0.025 \text{ V}}{8 \text{ fA} \cdot 10^{12} \Omega}\right) \approx 2.85 \times 10^{-2} \text{ V}
\end{aligned}$$

## Problem 7.

$$\begin{aligned}
r_\pi &= \frac{\beta_o V_T}{I_C} = \frac{100 \cdot 0.025 \text{ V}}{40 \mu\text{A}} = 62.5 \text{ k}\Omega \\
g_m &= \frac{I_C}{V_T} = \frac{40 \mu\text{A}}{0.025} = 1.6 \times 10^{-3} \Omega^{-1} \\
r_o &= \frac{1}{g_o} = \frac{V_A + V_{CE}}{I_C} = \frac{75 \text{ V} + 10 \text{ V}}{40 \mu\text{A}} = 2125 \text{ k}\Omega
\end{aligned}$$

$$R_L = r_o \parallel R_C \parallel R_3 \approx 48.85 \text{ k}\Omega$$

The input resistance is

$$R_B \parallel r_\pi \approx 38.46 \text{ k}\Omega$$

The voltage gain is

$$\begin{aligned} A_v^{CE} &= -g_m R_L \left[ \frac{R_B \parallel r_\pi}{R_I + (R_B \parallel r_\pi)} \right] \\ &= -1.6 \times 10^{-3} \Omega^{-1} \cdot 48.85 \text{ k}\Omega \cdot \left( \frac{38.46 \text{ k}\Omega}{750 \Omega + 38.46 \text{ k}\Omega} \right) \\ &\approx 76.7 \text{ dB} \end{aligned}$$