

---

UM-SJTU JOINT INSTITUTE  
ELECTRONIC CIRCUITS  
(VE311)

---

LABORATORY REPORT

LAB 1

Name: Chao Junyu  
Name: Liu Yihao

ID: 515370910206  
ID: 515370910207

Date: 17 June 2017

# Contents

<b>1</b>	<b>Objectives</b>	<b>3</b>
<b>2</b>	<b>Experiment procedures</b>	<b>3</b>
2.1	Resistor behavior . . . . .	3
2.2	Capacitors . . . . .	3
2.3	Array of resistors . . . . .	3
<b>3</b>	<b>Experimental results and discussion</b>	<b>4</b>
3.1	Resistor behavior . . . . .	4
3.2	Capacitors . . . . .	6
3.3	Array of resistors . . . . .	8
<b>4</b>	<b>Reference</b>	<b>9</b>
4.1	References . . . . .	9

## 1 Objectives

- Test the behavior that the resistance has to temperature, humidity, high current and voltage.
- Understand what happened when a series of capacitors behave at different conditions.
- Analyze the behavior of a simple array of resistors.

## 2 Experiment procedures

### 2.1 Resistor behavior

We are going to test the behavior that the resistance has to temperature, humidity, high current and voltage. By using a resistor of  $220\ \Omega$ ,  $10\ \text{k}\Omega$  and the closest to  $1\ \Omega$ , perform the follow set of tests.

- By using a wave generator and an oscilloscope, measure the resistor response for a voltage of 1, 5, 10 and 15 V by sweeping the frequency from 10 Hz up to 50 MHz in each case.
- In each case heat or warm the resistance and see if there is any change in the oscilloscope signal.
- “Carefully” reduce the temperature of the resistance and see what happen to the signal.

### 2.2 Capacitors

The second part considers the use of capacitors. In here, we are going to use a series of capacitors and to understand what happened when they behave at different conditions.

- Use the capacitors:  $3.3\ \mu\text{F}$ ,  $0.082\ \mu\text{F}$  and  $5\ \text{pF}$ . Each one of the capacitors is to be in series with a  $10\ \text{k}\Omega$  resistor. By applying  $1\ V_{pp}$  you’re going to sweep the frequency ranging from 50 MHz or the highest to 60 Hz.
- Invert the order of the devices and perform the same test.

### 2.3 Array of resistors

Finally, with an inductor, we are going to perform a set of experiments. By using a simple array of a  $10\ \text{k}\Omega$  resistor in series with an inductor, we’re going to analyze the behavior of the array. By using the wave generator, we are sweeping a range of frequencies from 50 MHz up to 1 Hz with a  $1\ V_{pp}$ .

## 3 Experimental results and discussion

### 3.1 Resistor behavior

We use the 10 k $\Omega$  resistor, which has the most apparent behavior. The voltage figure for the origin resistor was shown in Figure 1.

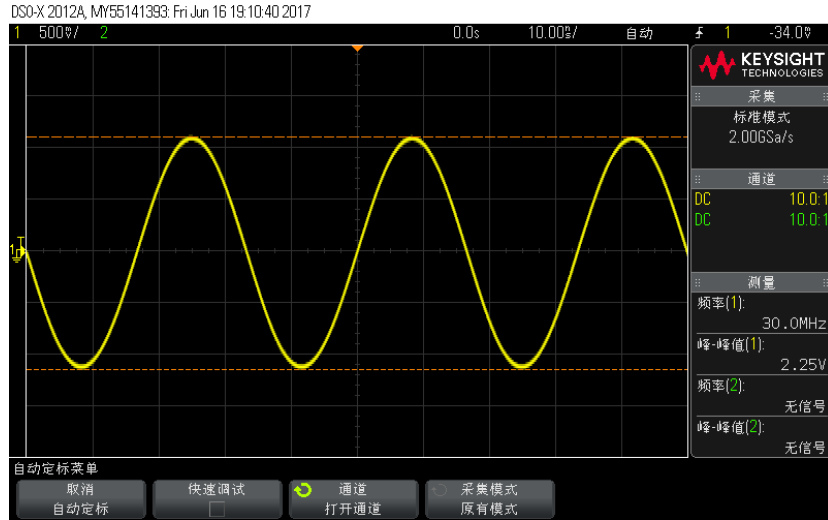


Figure 1: Origin voltage figure of  $R = 10\text{ k}\Omega$

When the temperature was raised, the comparison of the origin figure and the new figure was shown in Figure 2.

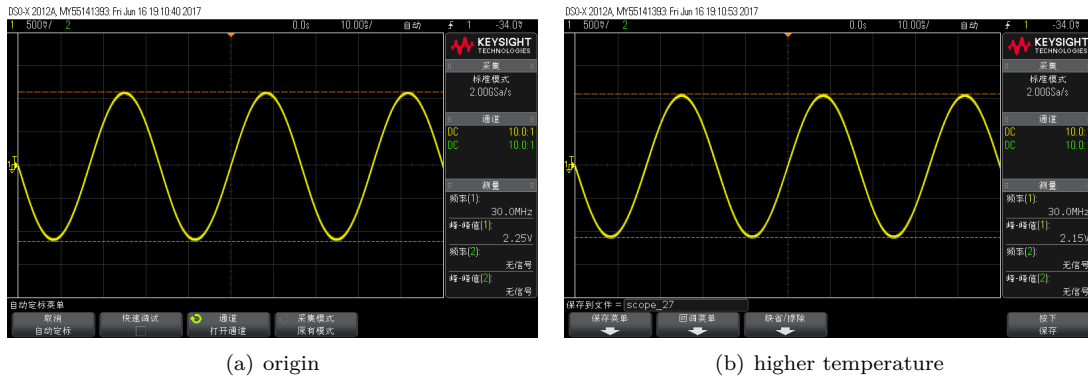


Figure 2: Comparison between origin figure and higher temperature

We can find that when the temperature rises, the voltage on the source become slightly higher, which means that the resistance becomes higher.

When the humidity was raised, the comparison of the origin figure and the new figure was shown in Figure 3.

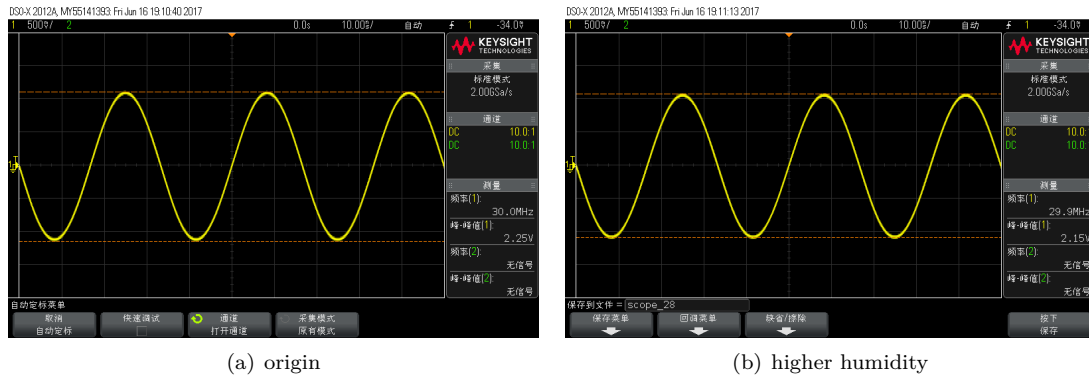


Figure 3: Comparison between origin figure and higher humidity

We can find that when the humidity rises, the voltage on the source become slightly higher, which means that the resistance becomes higher.

### 3.2 Capacitors

We choose two capacitors,  $3.3\mu\text{F}$  and  $0.082\mu\text{F}$ .

For the  $3.3\mu\text{F}$  capacitor, the figure was shown in Figure 4.

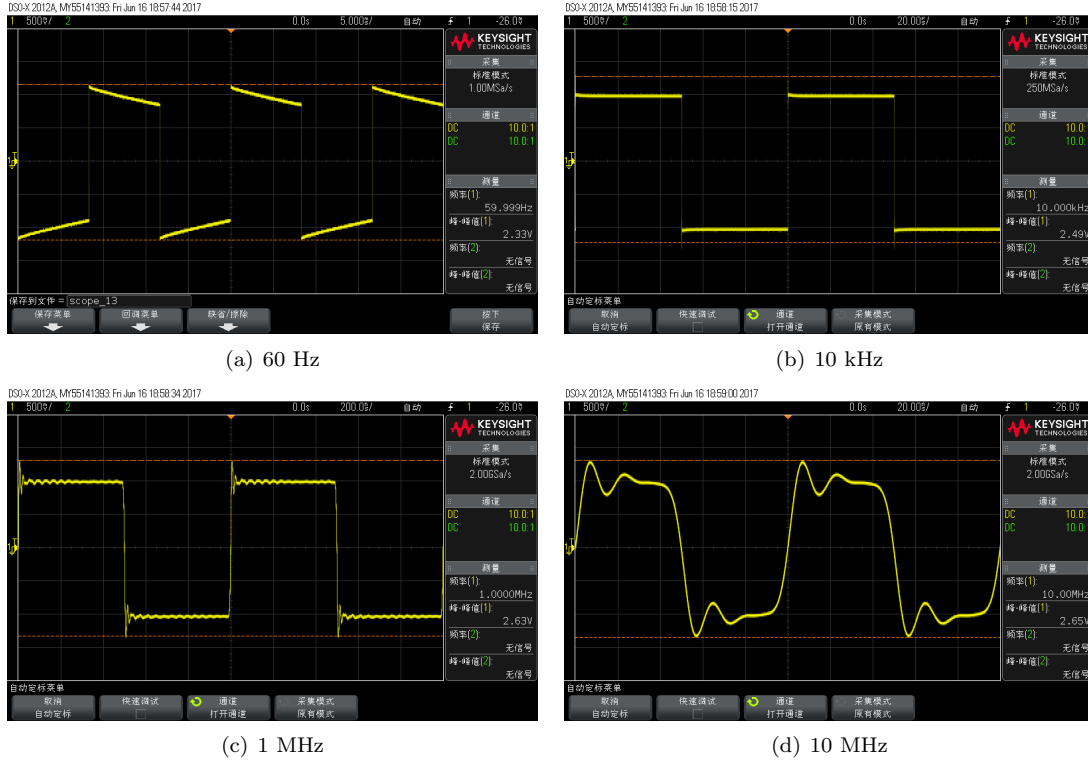


Figure 4:  $3.3\mu\text{F}$  capacitor

For the 0.082  $\mu$ F capacitor, the figure was shown in Figure 5.



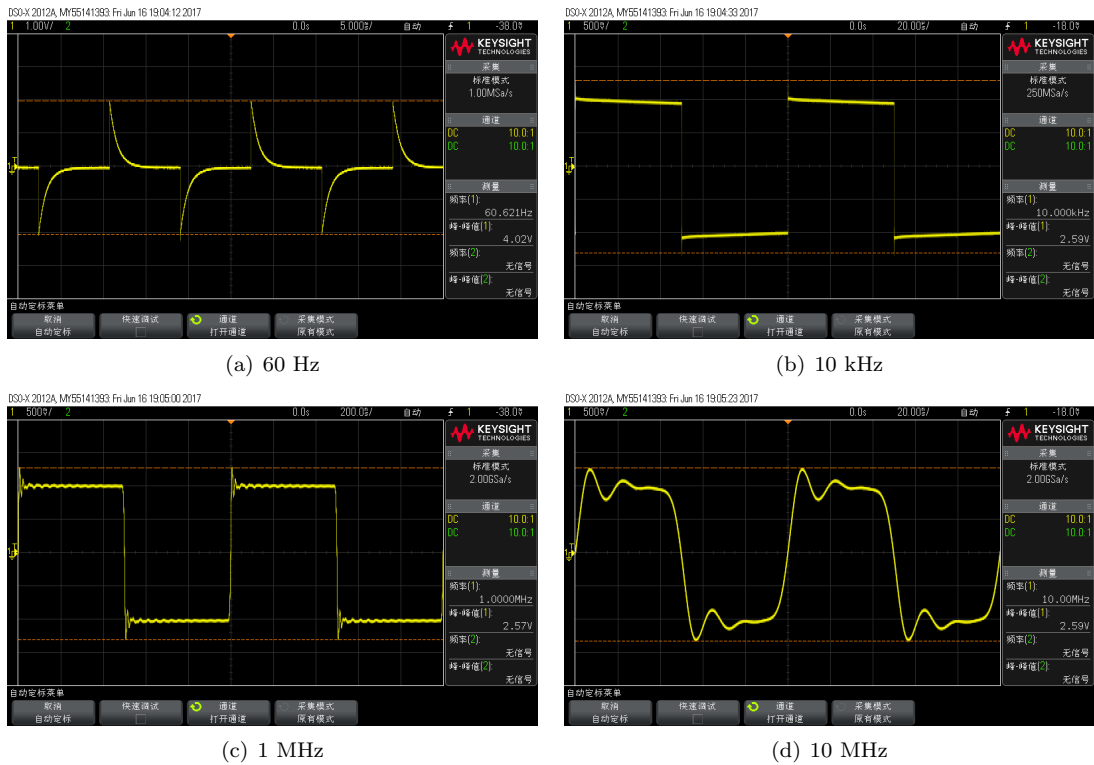


Figure 5: 0.082  $\mu$ F capacitor


### 3.3 Array of resistors

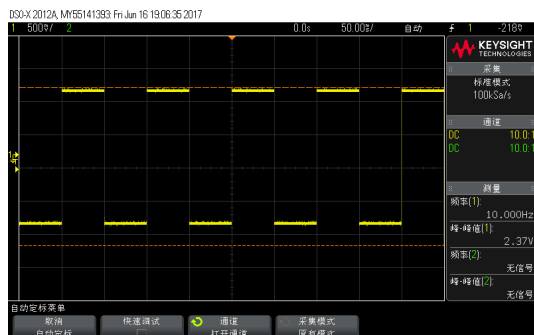


(a) 10 Hz

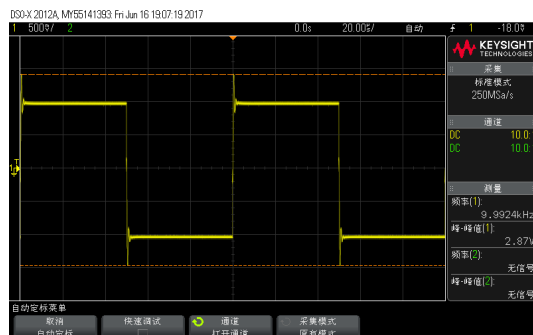

(b) 10 kHz

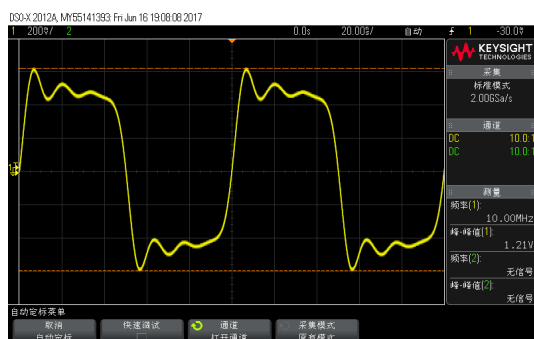

(c) 10 MHz

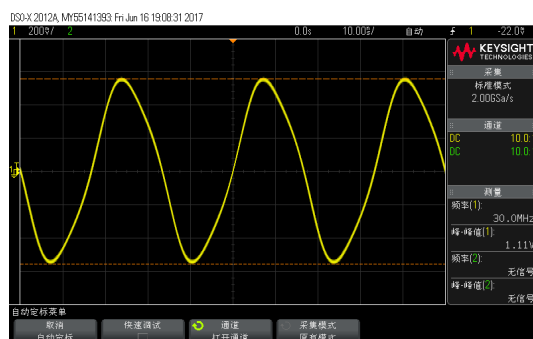

(d) 30 MHz

Figure 6: 0.082  $\mu$ F capacitor



## 4 Reference

### 4.1 References

1. Lab1 Manual